

100W VSFF PWM And HF CCM/QR USB PD Adapter Solution

Value Proposition

This design used Onsemi's NCP1623A PFC and NCP1343 HF CCM/QR Flyback PWM controller plus GAN mosand NCP4307 synchronous rectified controller combining Onsemi's WT6633 PD controller for 100W USB PD adapter.

Specifications and Features

- AC input from 90V to 264V i,
- VSFF CRM PFC with 2 stage output voltage, 250V at LL and 390V at HL н.
- HF CCM/CRM PWM with 2x PEM supports more power transition without PFC ÷. working and 68uF PFC capacitor
- High Frequency Operation up to avg. 190KHz at 264Vac&full load and easy to be changed to GaN solution
- Quite skip and Flyback DCM operation with frequency foldback at no load&light load
- Output voltage 3.3V-21V
- Max Output power: 100W
- Support PD3.0, PPS, BC1.2 etc.
- Ripple&Noise: <60mV
- AVG efficiency:93 % at 115Vac&230Vac
- Full load efficiency: 93%&93.5% at 115Vac&230Vac and 20V3.25A Output precise OVP
- Output OCP, SCP
- Open loop protection
- Small size with compact design ÷.
- PCBA size: 60mmx60mmx19mm ÷.
- Adapter size: 65mmx65mmx28mm

Market & Applications

- Mobile phone Quick Charger
- Laptop computer ÷.



Internal Use Only

Demoboard Photo









Schematic(PFC Portion)



_

UN

Schematic(PWM&Protocal Portion)

4





COC V5 Tier2 Specification and Average/Light Load Efficiency



avg efficiency Vs COC V5 Tier2

10% efficiency Vs COC V5 Tier2



5 5



Standby Power



6 0805/2021











115Vac and 20V5A

8

ON

Input Current at LL and HL



9 0805/2

0805/2021



PFC Operation Waveform at LL and HL



10

0805/2021



PFC LL to HL and HL to LL Change



11 0805/2021

Internal Use Only

ON.

PD Voltage Change



12 0

0805/2021



Ripple at 90Vac



ON

Output Ripple at 90Vac and 20V2.5A(Max Load Before PFC work)



ON

14

PWM Operation Frequency



15 08

0805/2021



Syn. Drive During Load Transition at 264V

264Vac and 15V, 0-3A

Tek Pre Tek Ϋ́ Zoom Factor: 50 X Zoom Position: 137µs Zoom Factor: 50 X Zoom Position: 4.41ms Vds-sec Vds-sec i a ta la interne Vsyn-drv 12 May 2021 16:35:10 250MS/s 5M points) Z 40.0µs , ↓ ▼1.20 250MS/s 5M points) Z 40.0µs **∏→▼**1.20 12 May 2021 16:36:08 3) / 50.0 V <mark>3)</mark> / 50.0 V

264Vac and 15V, 3A-0

16 080

0805/2021



NCP1343 Transition Load from 0-5A at 90Vac and 20V





Primary FET and SEC. FET Stress at 264Vac&Full load Normal operation, 264Vac, 20V5A Tek Stop Primary Vds: 596V Secondary Vds: 81V $\mathbb{1}$ 2.50GS/s 5M points 4.00μs **∎→▼**0.000000 s <mark>1</mark> / 592 V 1 100 V 4 Std Dev 1.867 10 May 2021 10:30:39 Mean 594.9 Min 592.0 Max 596.0 Value 1) Max 592.0 V

18

0805/2021



Pri.&Sec. Vds and Synchronous Drive Waveform



19

0805/2021



Short Circuit Protection and Tovld, Tauto-recovery time



20

0805/2021













X2 Capacitor Discharge Test



ON

264Vac and no load

23

EMI Test at 230Vac&Full Load





EMI TEST REPORT

Nature

24

0805/2021

EMI Test at 115Vac&Full Load





Line

25









Thermal Camera(PCBA Test)

90Vac&20V5A

115Vac&20V5A

230Vac&20V5A

230Vac&20V5A



26

0805/2021



PFC Inductor Specification



27

0805/2021

Transformer Specification



Internal Use Only

0805/2021 28

Summary

- > 2 stage PFC output and improve the efficiency at low line
- > 2x PEM controller supports more large power transition while PFC starts to work at some power
- > Comparing with QR controller, 68uF PFC capacitor is enough, so minimize capacitor's size and reduce cost



0805/2021

